

TG3: Analog Electronics for Ge detectors

Goal of Task Group: Delivery of

- Front-end (FE) circuits for Ge det. read-out
- Cables from FE to FADC
- HV-PS, LV-PS, Pulser
- Slow-control of operational parameters of digital and analog electronics.

Status of TG3 works: FE not ASIC cryogenic circuits

	Status / meet specs	Date	Notes
Test of FE Circuit 1 (AGATA, discrete components)	Achieved	09/05	Discrete components. Warm outside LN bath with cold FET
Test of FE Circuit 2 (IPA4 – monolithic JFET+ polarizing components)	Achieved	02/2005	Semi-integrated. Polarizing components, CF,RF not integrated.
Production of 20 FE channels for Ge prototypes at LNGS and MU	Achieved	05/2006	
Test of produced channels	To be done	07/2006	
Test of FE circuit 3 (AMPTEK- A250)	✓	12/2005	Ibrid can work at cryo-T.

Status of TG3 works: ASIC FE cryogenic circuits

MI- ASIC – CMOS FE			Integrated but not CF,RF
Test	Achieved	06/2005	
Test of chips	Achieved	12/2005	
2 nd run (fine tuning)	To be done	10/2006	
Production	To be done	2007	
MI- ASIC – CMOS FE			Fully Integrated but not RF, with possible active reset
Test run	Submitted	07/2006	
Test of chips	TBA	09/2006	
2 nd run (tuning)	TBA	10/2006	
Packaging	Candidate	04/2006	
Hd ASIC-CMOS			Fully integrated
Test run	Done	02/2006	
Test of chips	TBA	?	
2 nd run	TBA	?	
Production	TBA	2007	



Status of TG3 works : Cables (Phase I) and LV,HV PS

	Status / meet specs	Date	Notes
HV for Ge detector Caburn Kapton 8 kV 0,25 mm diam	Achieved	06/05	Measured by M.Laubenstein < 10 mBq/kg both for U and Th. (30 g/ 6 m)
Signal (from FE to FADC) and LV PS (picocoax-Axon) (siltem coax) (Tekdata woven)	X Ongoing, candidates exists	12/2005 05/2006	To be measured γ - spectrometry
LV PS	Candidate	07/2006	INFN-PD design and production
HV PS	Candidate		
Pulser	X	12/2006	

Possible problems

Too high radioactivity of components, as the junction box has to be put nearest the top of the crystal string compared to the showed solution (see talk of B.Majorovits)





IPA4+external FET BF862: Why?

 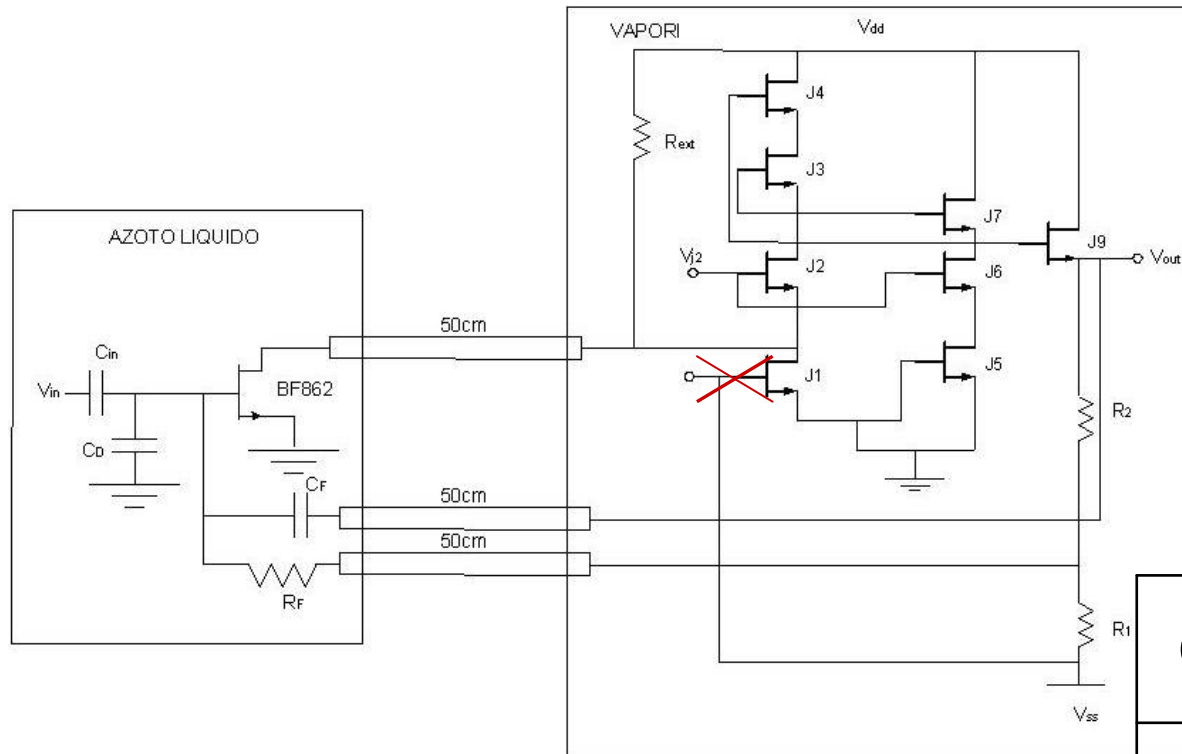

CD [pF]	τ_f [ns] (BF862)	τ_f [ns] (J1)
0	27	110
15	36	140
27	44	155

IPA4+external FET BF862 @ 300 K

  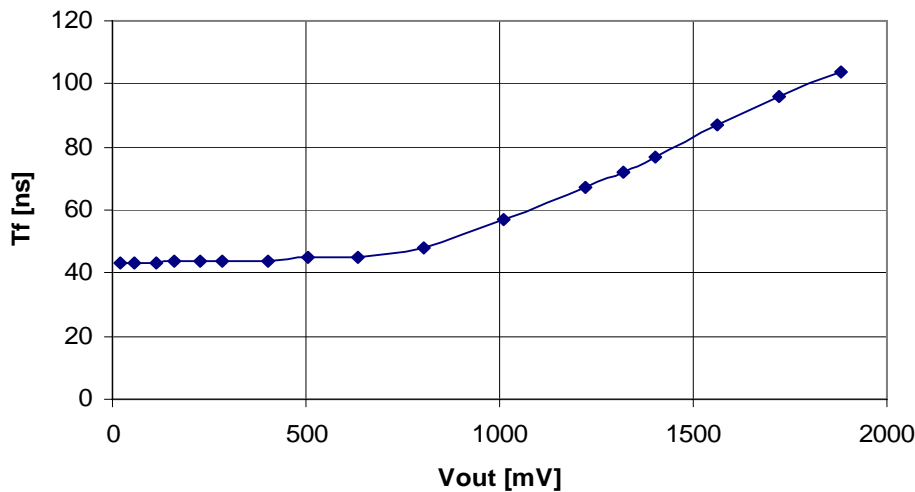 
Linearità $\frac{V_{out}}{Q_{in}} = 1,15V / pC$



17 Nov 2005 02:10:02


18 Nov 2005 02:02:18

IPA4+BF862_{ext} @ LN

 


IPA4+J1_{int}

VG=+12V VD=-4,5V

 


IPA4 + J1_{ext} + 100 Ω Out stage:
the new test board

New setup for LN measurements

 


 
IPA4 + J1_{ext} + 100 Out stage:
 simulated pulse 50 ns fall time (@ 300 K).




Swing to -1.5 V

IPA4 + J1_{ext} + 100 Ω Out stage:
the new test board

New setup for LN measurements

 
 


 Back to 1 k Ω out stage,
better pulse shape



Measured pulse fall time for IPA4 preamp. Operated with integrated J1 or external BF862, at T = LN.

CD [pF]	τ_f [ns] (BF862)	τ_f [ns] (J1)
0	27	110
15	36	140
27	44	155

  


Production of 20 FE cryogenics circuits (based on IPA4 JFET monolithic circuit) for MU 18 fold segmented prototype, and for LNGS Phase I detector tests

Production of PCB: 23 june at AREL, without 100 Ω output stage: Lowest dissipation and not perfect shape

Mounting of components: this week (end 30 june provided I send components).

For LNGS test: 2-3 channels

 
For MU 18-fold crystal: test and mount circuits on mother board to host 20 preamps and signal-in signal-out. Ready to work end-july.



IPA4+BF862 LC POS SCALA 1:1 08/05/06



 80\20\80 1:1 AJA2 209 2J 8878++AI IPA4+BF862



IPA4+BF862 LC POS SCALA 1:1 08/05/06

S. Riboldi, A. Pullia, F. Zocca, C. Cattadori

Charge Preamplifier and
Fully Differential Line Driver
Integrated in AMS CMOS 0.8um CXZ Tech.
for the GERDA Experiment

Milan University and I.N.F.N.

Input transistor


External (JFET e.g. BF862)

- Noise is adequate
- Bandwidth is adequate
- Transistor can be replaced
- Can work at $V_{GS} = 0$ V which helps zeroing the output offset
- Power consumption is high


Integrated (p-MOSFET)

- Noise could be adequate
- Bandwidth is adequate
- Transistor cannot be replaced
- Transistor cannot work at $V_{GS} = 0$ V
- Power consumption of p-MOSFET could be lower

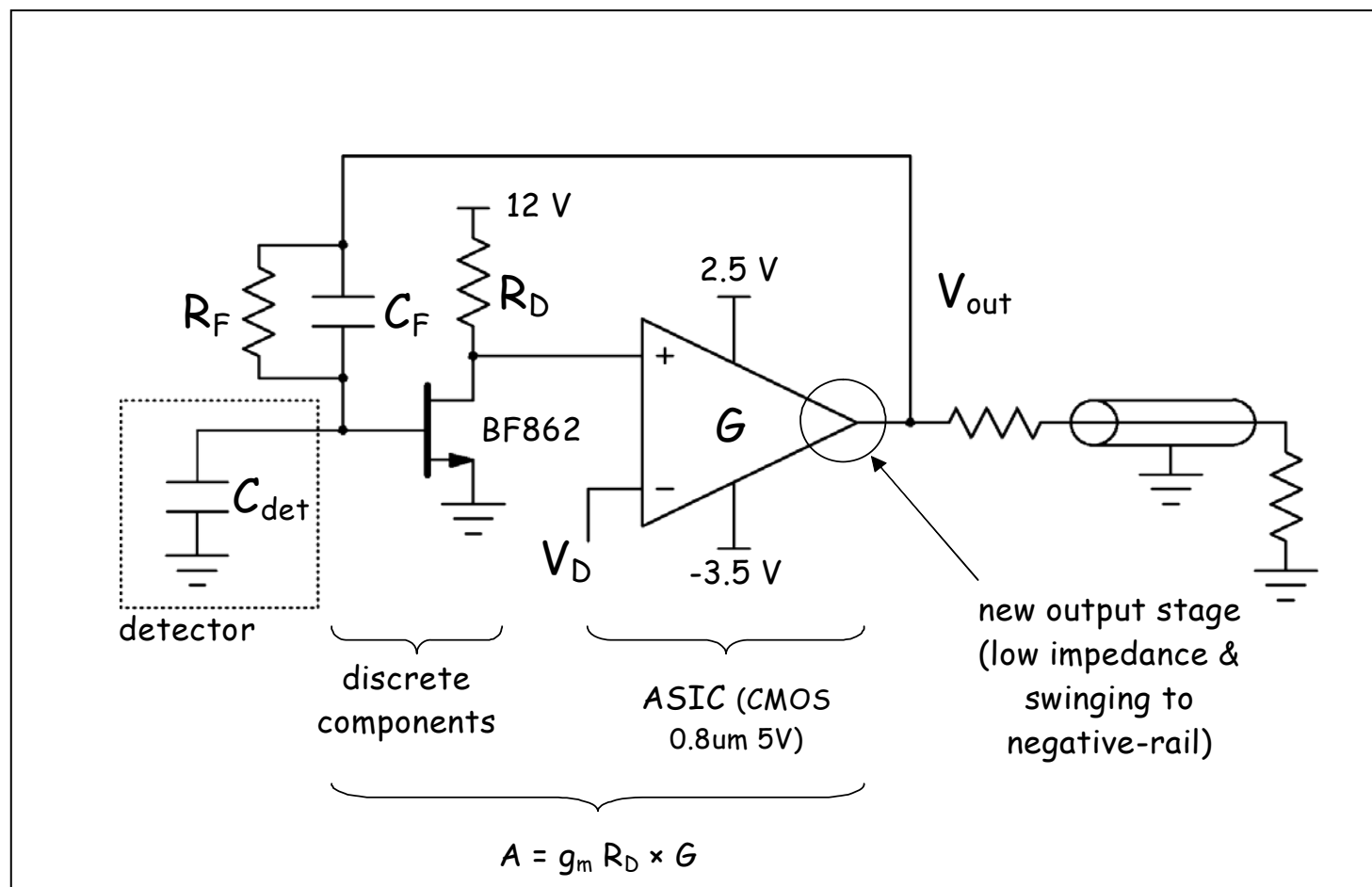
Proposed circuit structure (from J. Gal*)



Test chip

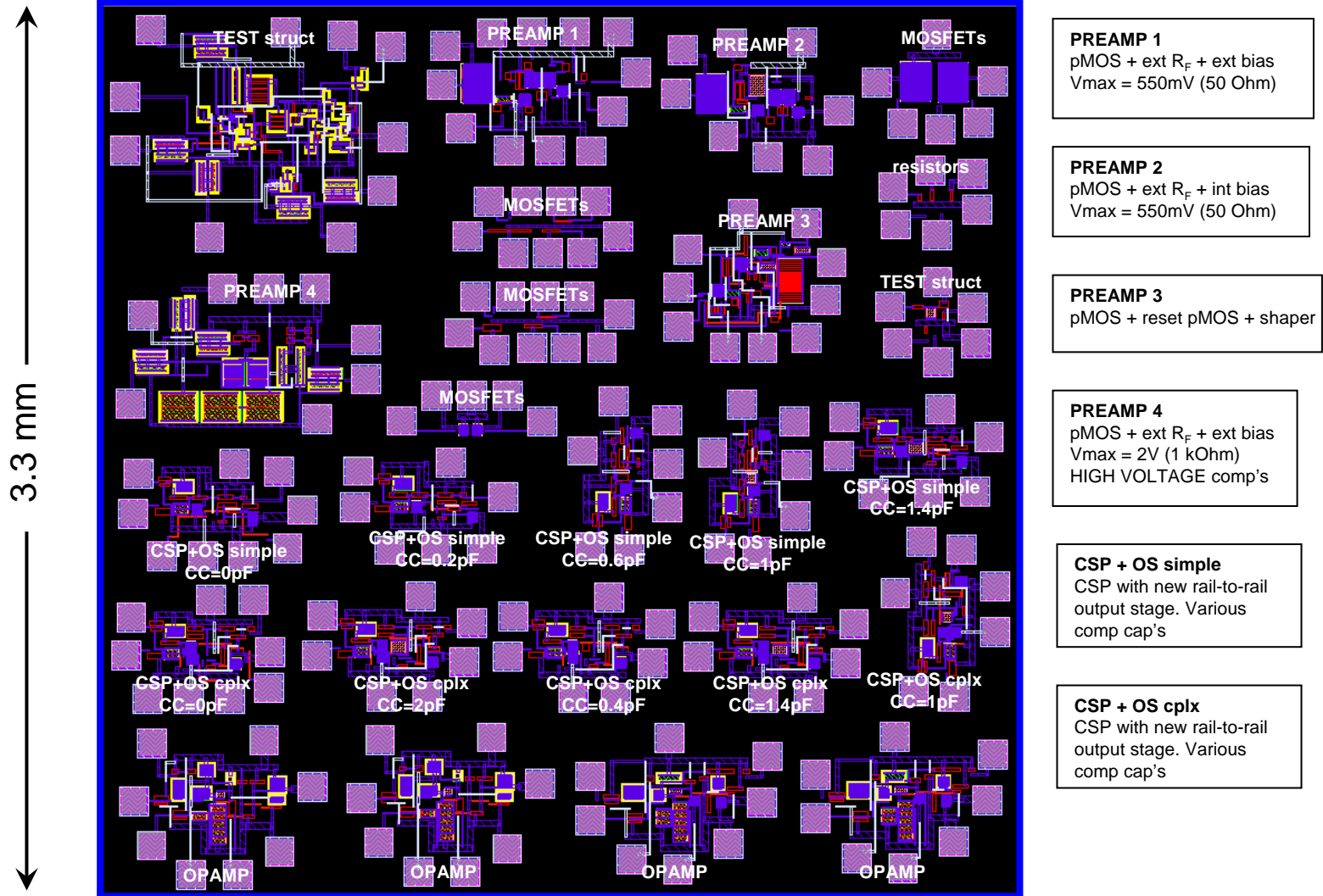

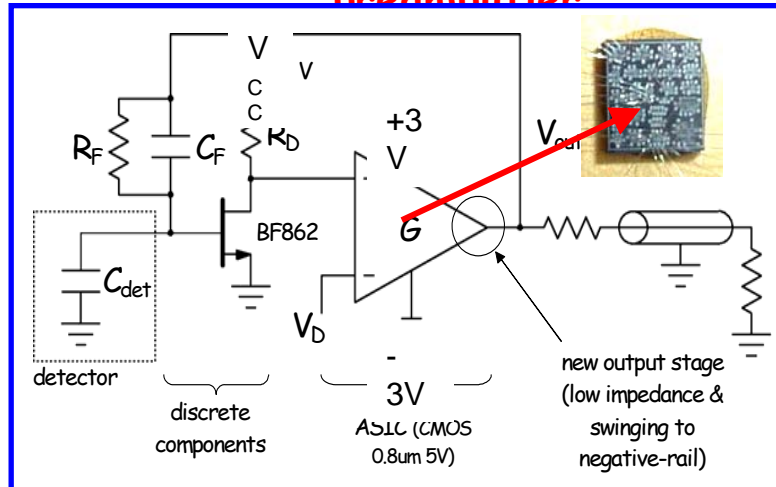Tested circuit structure: external BF862 JFET + 0.8 μ m 5V CMOS single-ended preamplifier




First measurement results at T=77°K

($C_F = 0.15\text{pF}$, $R_F = 1\text{G}\Omega$, $C_{\text{det}} = 15\text{pF}$)


- Negative output voltage swing: $\sim 2.4\text{ V}$
- Energy sensitivity ($C_F = 0.15\text{ pF}$): $\sim 185\text{ mV/MeV}$ after $50\ \Omega$ termination
- Input dynamic range: $\sim 6.5\text{ MeV}$
- Rise time: $\sim 15\text{ ns}$ driving 10m cable
- Minimum ENC ($C_{\text{det}} = 15\text{pF}$): 112 e^- at $\tau_{\text{shap}} = 10\ \mu\text{s}$
- Total power consumption: $\sim 25\text{ mW}$

GERDA meeting 26-28 June 2006

 
Acquired output signal driving a 50 Ω coaxial cable of $\sim 10\text{ m}$: rise time of $\sim 15\text{ ns}$



 Comparison between noise measured at room temperature ($T=300^\circ\text{K}$) and in LN ($T=77^\circ\text{K}$)




Integrated Preamplifier

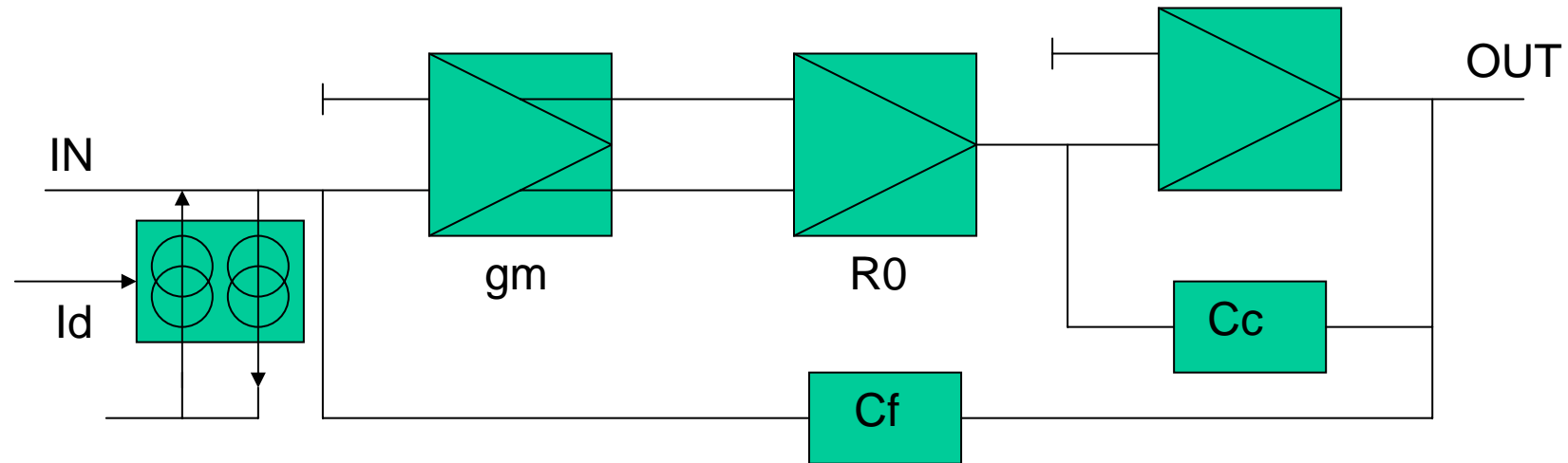

- Tunable system (variable g_m and R_0 by a factor of 10)
- Noise, bandwidth according to specifications
- Dual Power Supply (+2.5v / -2.5v) / No additional Vrefs required
- Fully Bipolar Output Swing (+1.6v / -1.6v) @ $R_{load} = 1 \text{ Kohm}$
- Non linearity $< 1/1000$ @ (-1.6v $<$ Output Swing $<$ +1.6v)
- Can operate with continuous reset (external R) or pulsed reset (bipolar Id)

Fully Differential Line Driver

 

Fully Differential Line Driver

- Dual Power Supply (+2.5v/-2.5v)
- No additional Vrefs required
- Fully Differential Signal Path inside the OpAmp
- Fully Bipolar Output Swing (+2v/-2v) @ Rload = 100 Ohm
- Large Differential Output Swing (8v) @ Rload = 100 Ohm
- Bandwidth according to specifications
- Tunable system
- Variable Power Consumption:
(from 3 mA @ Low Power up to 6 mA @ Full Bandwidth)

Low Voltage Low Noise PS designed at PD –INFN workshop
($V=+12\text{ V}$, $V=+5\text{ V}$, $V=-5\text{ V}$, $I = 0.7\text{ A}$ each)

If test OK then can be adopted for
GERDA

